

Newton's Law of Cooling

T_s = temperature of surroundings

$T(t)$ = temperature at time t .

$$\frac{dT}{dt} = k(T - T_s) \quad \text{where } k < 0.$$

Method 1. $\int_{T-T_s} \frac{dT}{T-T_s} = \int k dt$

Method 2. let $u = T - T_s$ then $\frac{du}{dt} = \frac{dT}{dt}$

$$\frac{du}{dt} = k(T - T_s) = ku \quad \therefore u(t) = u(0) e^{kt}$$
$$u(0) = T_0 - T_s$$

Example Temperature in Fridge is 7°C

Dinner at room temperature is 22°C .

After 30 min in the fridge, dinner

is now 16°C , Solve for k .

A First Order linear ODE (FOPE)

is an ODE of the following form:

$$\frac{dy}{dx} + P(x)y = Q(x), \quad \text{where } P(x), Q(x) \text{ are given functions of } x,$$

$$\frac{dy}{dx} = Q(x) - P(x)y = F(x, y) \quad \text{This is not separable}$$

unless $P(x) = a Q(x)$ where a is a constant.

To solve this we use an integrating factor

$$G(x) = e^{\int P(x) dx} \quad \text{then} \quad G'(x) = P(x) e^{\int P(x) dx} = P(x) G(x)$$

$$\begin{aligned} \frac{d}{dx} (y G(x)) &= \frac{dy}{dx} G(x) + y P(x) G(x) \\ &= G(x) \left(\frac{dy}{dx} + y P(x) \right) \\ &= G(x) Q(x) \end{aligned}$$

$$\therefore y G(x) = \int G(x) Q(x) dx + C$$

$$y = \frac{1}{G(x)} \left(\int G(x) Q(x) dx + C \right)$$

Example $y' + \frac{1}{x}y = 7$

$$P(x) = \frac{1}{x} \quad Q(x) = 7$$

$$G(x) = e^{\int \frac{1}{x} dx} = e^{\ln|x|} = |x|$$

These are usually populations, so if \mathbb{R} assumed $x > 0$,

$$G(x) = x$$

$$y = \frac{1}{x} \left(\int x + 7 \cdot dx + C \right) = \frac{1}{x} \left(\frac{7x^2}{2} + C \right)$$

$$= \frac{7x}{2} + \frac{C}{x}$$


Ex $y' + 3x^2y = 7x^3$

(separable).

$$P(x) = 3x^2 \quad Q(x) = 7x^3$$

$$G(x) = e^{\int 3x^2 dx} = e^{x^3}$$

$$y = 1$$

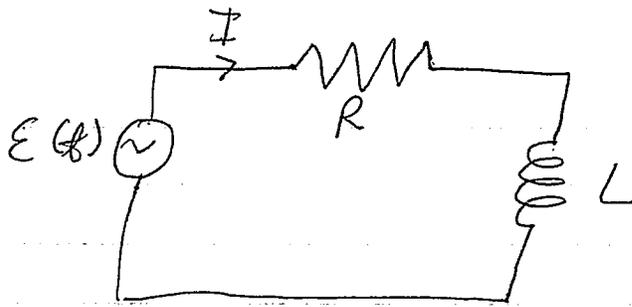

R = resistance in ohms
 L = inductance in henrys
 $E(t)$ = electromotive force in volts
 $I(t)$ = current in amps

Kirchoff's Voltage Law: The directed sum of electrical potential differences around any closed circuit is zero.

$$IR + L \frac{dI}{dt} = E(t)$$

$$\frac{dI}{dt} + \left(\frac{R}{L}\right)I = \frac{E(t)}{L}$$

If R and L are not time dependent (independent of t), then the integrating factor is,

$$e^{\int \frac{R}{L} dt} = e^{(Rt)/L}$$

$$\therefore I = \frac{1}{e^{(Rt)/L}} \left(\int e^{\frac{Rt}{L}} \frac{E(t)}{L} dt + C \right)$$

$$= \frac{e^{-(Rt)/L}}{L} \int e^{\frac{Rt}{L}} E(t) dt + C e^{-\frac{(Rt)}{L}}$$

$C e^{-\frac{Rt}{L}}$ is called a transient as it goes to 0 as $t \rightarrow \infty$.